


Makenzie Brian

October 2, 2015

ECE 272

Lab 4 Study Questions

Block Diagram: (ish)

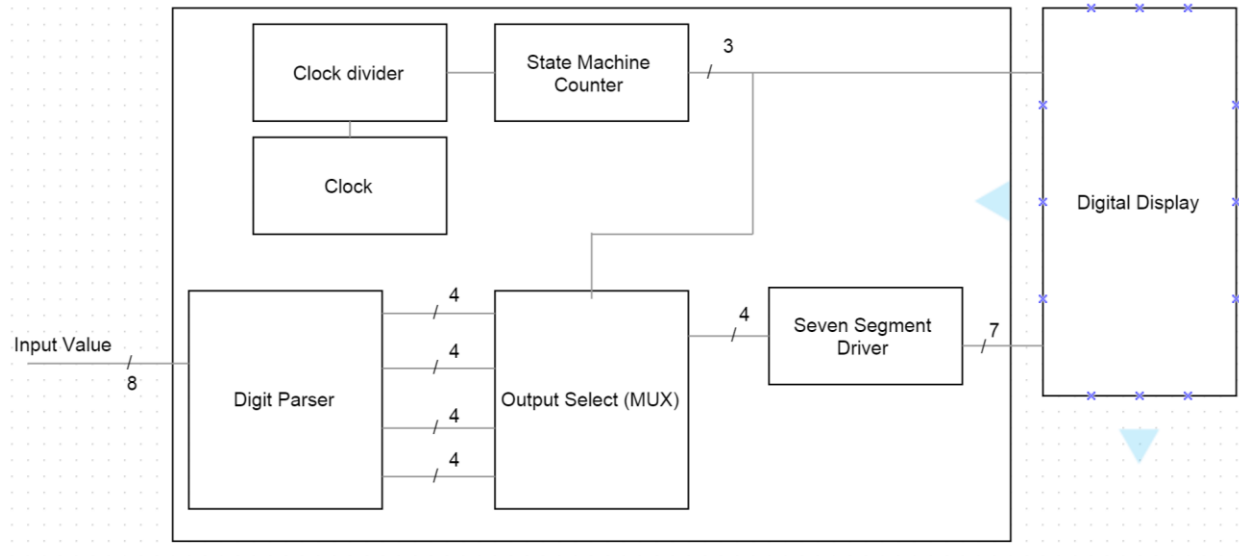

Pins:40-47 and 56-58 to pins: A-G and SEL 0-2

GND to GND,PWM, EN_N

3.3V to EN, VDD

Schematic:

